# Stream Syncer

A small SystemVerilog project by Naftali Kizner © 2021

# **Challenge Definition**

Imagine an endless incoming bit stream, divided into frames of fixed length (e.g., 128 bits) with a fixed 8-bit beginning pattern (e.g., 11101000 ('he8)). 3 consecutive appearances of this pattern (one per frame) should be found to declare in-frame. The data is output as an 8-bit bus.

### Task Breakdown


Interface will be defined as follows, with a few assumptions taken:

Name	I/O	Duty
stream	Input	Endless bit stream
clock	Input	Clock
reset	Input	Reset the machine
data_out[7:0]	Output	Filtered buffered data (w/o pattern)
data_valid	Output	data_out is valid for reading
in_frame	Output	data_out is within a legal frame

This system is looking for 3 legal frames, meaning frames that begin with a specific sequence, to declare a legal data output. Any discovery of this sequence out-of-sync, meaning not every frame length, will be handled by resyncing.

 
# Solution

The system consists of two shift registers, a controller (FSM), a comparator, a frame-size counter, and other combinational logic. Top-level diagram is shown below:



The usage of two shift registers allows flexibility of the output bus size, meaning the system is capable of dealing with sequence sizes which are different from the output bus size.
 
#### The FSM is described by the state diagram below:



#### Controller's pseudo state table is given below:

Current State	Next state			data_valid				in_frame				
	pattern on time	early pattern	late/no pattern	data frame	pattern on time	early pattern	late/no pattern	data frame	pattern on time	early pattern	late/no pattern	data frame
no_sync	ptrn1	ptrn1	no_sync	no_sync	0	0	0	0	0	0	0	0
ptrn1	ptrn2	ptrn1	no_sync	ptrn1	0	0	0	0	0	0	0	0
ptrn2	in_sync	ptrn1	no_sync	ptrn2	0	0	0	0	0	0	0	0
in_sync	in_sync	ptrn1	no_sync	in_sync	0	0	0	1 every 8 cycles	1	0	0	1

#### Where inputs to the FSM are defined as:

• Pattern on time - is\_pattren == 1 && counter == 128

• Early pattern - is\_pattren == 1 && counter < 128


• Late/no pattern - is\_pattren != 1 && counter == 128

• Data frame - is\_pattern != 1 && counter < 128

# Results


Three tests comprise the testbench:

1. Streaming 4 proper frames

 


Results appear as expected: in frame rises after the 3rd pattern, and data valid strobes every 8 bits.

 2. Streaming one proper frame, then one short (by one byte), and then another 2 proper frames



Results appear as expected: in\_frame nor data\_valid ever rise.

 3. Streaming a frame that has an extra byte, then one short (by one byte), and then 4 proper frames



Results appear as expected: the system managed to sync and raise in\_frame and data\_valid properly.

# **Further Development**

Only 3 test scenarios were run on the system. More tests should be run, while altering the following parameters:

- Stream frames length
- Stream frames content
- Size of data out
- Sync pattern

### Code

Project's code is available at:

https://github.com/naftali10/Samll-SV-Projects/tree/main/Stream%20Syncer

It's also available for running at:

https://www.edaplayground.com/x/rxwh

Instructions for running:

Enter the link and press the Run button on the top-left corner. You will be asked to log in to EDA playground. Do so by clicking the orange "Log In (no save)" button. Choose your preferred login method - Google/Facebook account is good enough. Once logged in, re-enter the link above and click Run again. The log file at the bottom will display results of the testbench on the left.